

1. (30-59) No. If the entire moving conductor is in uniform \vec{B} , then $\frac{d\Phi_B}{dt} = 0$ and $\mathcal{E}_{ind} = 0$.

2. (30-64) $\vec{E} = (270 \frac{kV}{m \cdot s}) t (\hat{i} - 2\hat{j} + 3\hat{k})$

$$A_1 = \pi (0.65 m)^2 \quad \hat{n}_1 = \hat{k}$$

$$\begin{aligned} I_{d1} &= \epsilon_0 \frac{d\Phi_{E1}}{dt} = \epsilon_0 \frac{d}{dt} \left[\pi (0.65 m)^2 (270 \frac{kV}{m \cdot s}) t \cdot 3 \right] \\ &= (8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2}) \pi (0.65 m)^2 (270 \frac{kV}{m \cdot s}) \cdot 3 \\ &= \boxed{9.5 \times 10^{-6} A} \quad \text{direction } \boxed{+z} \end{aligned}$$

$$I_{d2} = \epsilon_0 \frac{d\Phi_{E2}}{dt} = \epsilon_0 \frac{d}{dt} \left[(0.50 m)^2 (270 \frac{kV}{m \cdot s}) t \cdot 1 \right]$$

$$(\text{Area } 2 = (0.50 m)^2 \hat{i})$$

$$I_{d2} = \boxed{6.0 \times 10^{-7} A} \quad \text{direction } \boxed{+x}$$

PHYS 230-01

3. (31-1)



$$V(t=0) = \frac{Q_0}{C}$$

$$V(t) = \frac{Q_0}{C} e^{-t/RC}$$

$$= \frac{0.27C}{6.0 \times 10^{-4} F} e^{-(6.0 \Omega) / [(6.7 \times 10^3 \Omega) \cdot (6.0 \times 10^{-4} F)]}$$

$$= \boxed{100V} \quad I = \frac{E}{R} = \frac{100V}{6.7 \Omega} = \boxed{15mA}$$

4. (31-4)

Solenoid: $N = 750$ $l = 2.5 \text{ cm}$ $r = 0.45 \text{ cm}$

$$L = \frac{\mu_0 N^2 A}{l} = \frac{(4\pi \times 10^{-7} \frac{T \cdot m}{A}) (750)^2}{(2.5 \times 10^{-2} \text{ m})} \pi (4.5 \times 10^{-3} \text{ m})^2$$

$$= \boxed{1.8 \text{ mH}}$$

5. (31-6)




$$N_p = 100 \quad N_s = 500$$

$$\Delta V_p = (100V) \cos \omega t$$

$$\Delta V_s = \left(\frac{N_s}{N_p}\right) \Delta V_p = \boxed{(500V) \cos(\omega t)}$$

6. (31-7)

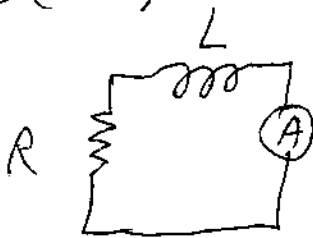

Discharging inductor:


$$I = I_0 e^{-t/\tau} \quad \text{with } \tau = \frac{L}{R}$$

$$I_0 = I e^{t/\tau}$$

$$= (0.050A) e^{4\mu / 1.33 \mu}$$

$$= \boxed{1.0A}$$
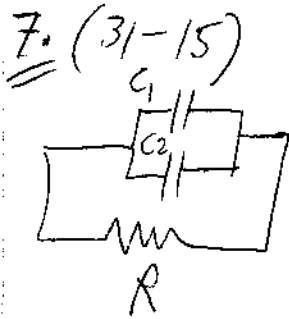
$$= \frac{4.0 \mu H}{3.0 \Omega} = 1.3 \mu$$



$$\tau = RC_p = R(C_1 + C_2)$$

$$R = \frac{\tau}{(C_1 + C_2)} = \frac{1.0 \times 10^{-3} \text{ s}}{(16 \mu\text{F} + 20 \mu\text{F})} = \boxed{28 \Omega}$$

8. (31-18)



Initial charge on capacitor is $Q_0 = EC$

Initial current after battery removed is


$$I_0 = \frac{AV_c}{R} = \frac{Q_0}{CR} = \frac{E}{R}$$

$$\text{Thus } R = \frac{E}{I_0} = \frac{12 \text{ V}}{0.24 \text{ A}} = \boxed{50 \Omega}$$

$$\text{At time } t = 3.0 \mu\text{s}, I = I_0 e^{-t/RC}$$

$$= \boxed{9.5 \times 10^{-2} \text{ A}}$$

9. (31-27)

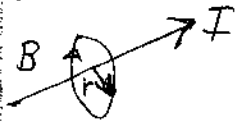

Ampere's Law


$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{through}}$$

$$2\pi r B = \mu_0 I \quad \text{or} \quad B = \frac{\mu_0 I}{2\pi r}$$

$$\mu_B = \frac{B^2}{2\mu_0} = \frac{\mu_0 I^2}{8\pi^2 r^2}$$

$$= \frac{(10^{-7} \frac{\text{T}\cdot\text{m}}{\text{A}})(8.0 \times 10^2 \text{ A})^2}{2\pi (5.0 \text{ m})^2} = \boxed{4.1 \times 10^{-4} \text{ J/m}^3}$$

10. (31-48)

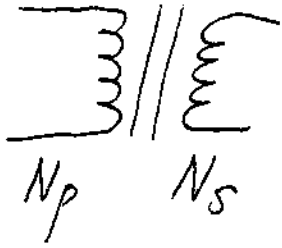

$$\text{Want } \frac{V_s}{V_p} = \frac{110V}{33V} = \frac{N_s}{N_p}$$

$$\text{Thus } \frac{N_s}{N_p} = \boxed{\frac{10}{3}}$$

(On-line homework looks for

$$\frac{N_p}{N_s} = \frac{3}{10}.)$$

This could be done with 3 turns on primary and 10 turns on secondary, or with $N_p = 33$ and $N_s = 110$.