

A. MULTIPLE-CHOICE QUESTIONS. CIRCLE THE BEST ANSWER.

(6 Pts. each):


1. A 5.0Ω resistor is in parallel with a 10.0Ω resistor as shown. What is the equivalent resistance between points A and B?

- a. 0.067Ω
- b. 0.30Ω
- c. 3.3Ω
- d. 7.5Ω
- e. 15Ω

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{5.0 \Omega} + \frac{1}{10.0 \Omega} = \frac{3}{10.0 \Omega}$$

$$R_p = 10.0 \Omega / 3 = 3.3 \Omega$$

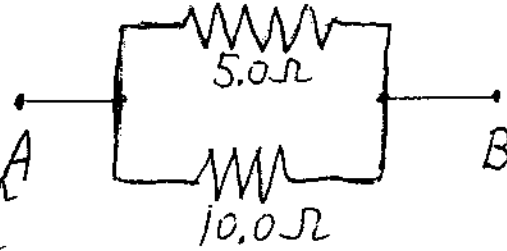

2. An 0.020 F parallel-plate capacitor with vacuum dielectric is attached to a 10V battery, allowed to fully charge, and then removed from the battery. A material with dielectric constant 4 is then placed between the plates. What is the stored energy in the capacitor with dielectric?

- a) 0.06 J
- b) 0.25 J
- c) 1 J
- d) 2.5 J
- e) 4 J

$$Q = CV = (0.02 \text{ F})(10 \text{ V}) = 0.2 \text{ C}$$

$$C' = KC$$

$$U = \frac{Q^2}{2C'} = \frac{(0.2 \text{ C})^2}{2(4)(0.02 \text{ F})} = 0.25 \text{ J}$$


3. A 20 A current flows in a circular loop of radius 0.1 m as shown. What is the magnetic moment of the loop?

- a. $2.0 \text{ A}\cdot\text{m} \hat{i}$
- b. $0.63 \text{ A}\cdot\text{m}^2 \hat{k}$
- c. $-0.63 \text{ A}\cdot\text{m}^2 \hat{k}$
- d. $-2.0 \text{ A}\cdot\text{m} \hat{i}$
- e. $0.2 \text{ A}\cdot\text{m}^2 \hat{k}$
- f. $-0.2 \text{ A}\cdot\text{m}^2 \hat{k}$

$$\vec{m} = IA \hat{n}$$

$$= \pi (0.1 \text{ m})^2 (20 \text{ A}) \hat{k}$$
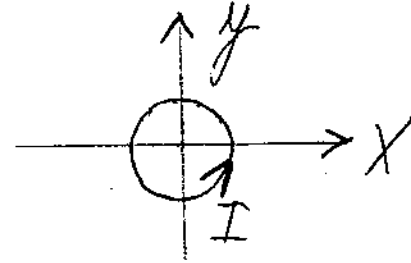
$$= 0.63 \text{ A}\cdot\text{m}^2 \hat{k}$$



4. The magnetic field in a region is given by $\mathbf{B} = (3 \text{ T}) \cdot (\hat{i} + \hat{k})$. A particle of charge 0.1 C with velocity $\mathbf{v} = 50 \text{ m/s} \hat{k}$ enters the region. What is the magnetic force on it?

- a) $15 \text{ N} \hat{j}$
- b) $-15 \text{ N} \hat{j}$
- c) $15 \text{ N} \hat{k}$
- d) $-15 \text{ N} \hat{k}$
- e) $7.5 \text{ N} \hat{j}$
- f) $-7.5 \text{ N} \hat{k}$

$$\vec{F} = q \vec{v} \times \vec{B}$$

$$= (0.1 \text{ C})(50 \frac{\text{m}}{\text{s}}) (3 \text{ T}) \hat{k} \times (\hat{i} + \hat{k})$$

$$= 15 \text{ N} \hat{j}$$

5. A wire segment of length 0.20 m lies along the x-axis and is centered on the origin. It carries a current of 5.0 A in the $-x$ direction. What is the magnetic field \mathbf{B} at the position $(x=0, y=0.12 \text{ m}, z=0)$?

- a. $8.3 \times 10^{-7} \text{ T} \hat{k}$
- b. $-8.3 \times 10^{-7} \text{ T} \hat{k}$
- c. $6.9 \times 10^{-6} \text{ T} \hat{k}$
- d. $-6.9 \times 10^{-6} \text{ T} \hat{k}$
- e. $6.9 \times 10^{-6} \text{ T} (0.71 \hat{i} - 0.71 \hat{j})$
- f. $-6.9 \times 10^{-6} \text{ T} (0.71 \hat{i} - 0.71 \hat{j})$

$$d\vec{B} = \frac{\mu_0}{4\pi} I \frac{d\vec{l} \times \vec{r}}{r^2}$$

$$= (10^{-7} \frac{\text{T}\cdot\text{m}}{\text{A}}) (5.0 \text{ A}) \frac{0.20 \text{ m}}{(0.12 \text{ m})^2} [-\hat{i} \times \hat{j}]$$

$$= -6.9 \times 10^{-6} \text{ T} \hat{k}$$


c b b a d

3

B. PROBLEMS. BE SURE TO SHOW YOUR METHOD CLEARLY. BE SURE THAT ANSWERS ARE WRITTEN IN TERMS OF ONLY GIVEN QUANTITIES.

1. Consider the circuit shown.

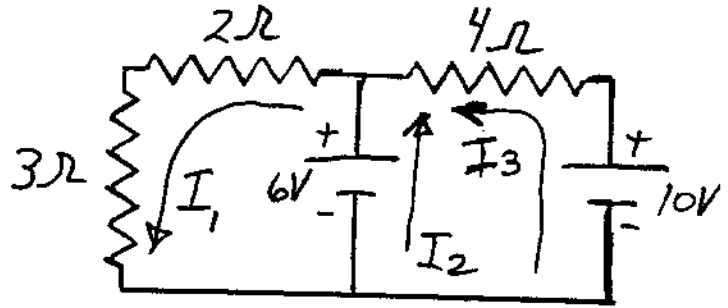a) Find the current I_1 ; be sure to indicate whether your value is positive or negative.



$$6V - I_1(2\Omega + 3\Omega) = 0$$

$$I_1 = \frac{6V}{5\Omega} = 1.2A$$

b. Find the value and sign of the current I_3 .

$$10V - I_3(4\Omega) - 6V = 0$$

$$I_3 = \frac{4V}{4\Omega} = 1A$$

c. How much power is dissipated in the 2 Ω resistor?

$$P = I_1 \Delta V \quad \Delta V = I_1(2\Omega)$$


$$P = I_1^2(2\Omega) = (1.2A)^2(2\Omega) = 2.9W$$

2. Consider the capacitor circuit shown.

a) What will be the charge on C_1 ?

$$Q_1 = C_1 \Delta V_1$$

$$= (2F)(10V) = 20C$$

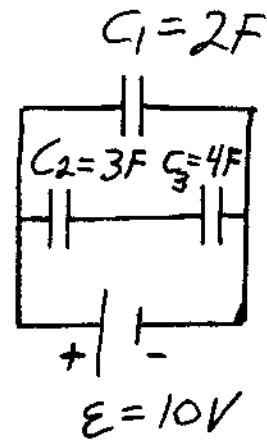

b) What will be the charge on C_2 ?

$$Q_2 = Q_3 = Q_5 = EC_5$$

$$\frac{1}{C_5} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{3F} + \frac{1}{4F} = \frac{7}{12F}$$


$$C_5 = \frac{12}{7}F$$

$$Q_2 = (10V)\left(\frac{12}{7}F\right) = 17C$$

What will be the potential difference across C_3 ?

$$\Delta V_3 = \frac{Q_3}{C_3} = \frac{17C}{4F} = 4.25V$$

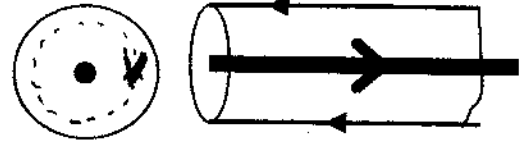3. Consider a long coaxial cable made with a central wire of radius 0.05m carrying a current of 5A surrounded by a cylindrical shell of radius 0.20 m. carrying current 5A in the opposite direction.



Cross-section

a) Draw in on the figure and describe the Amperian curve you would use to find the magnitude of the magnetic field at a radial distance of 0.15 m from the axis of the wire.

Circle of radius 0.15m around the wire axis

b) What is the magnitude of the magnetic field at a radial distance of 0.15 m from the axis of the wire? Be sure to show your method!

$$\mathcal{C} = 2\pi r B = \mu_0 I_{\text{through}}$$

$$B = \frac{\mu_0 I_{\text{through}}}{2\pi (.15\text{m})} = \frac{(4\pi \times 10^{-7} \text{T}\cdot\text{m/A})(5\text{A})}{2\pi (.15\text{m})}$$

$$= 6.67 \times 10^{-6} \text{T}$$

c) What is the magnetic field magnitude outside the cable at a radial distance 0.30m from the axis? Be sure to show your method!

$$2\pi r = \mu_0 I_{\text{through}} = \mu_0 (+5\text{A} - 5\text{A}) = 0$$

$$\underline{B=0}$$