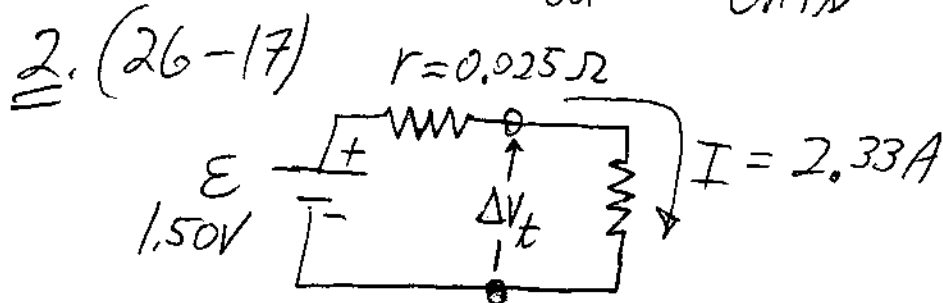



Phys 230

# SOLUTIONS - PROB. SET 5

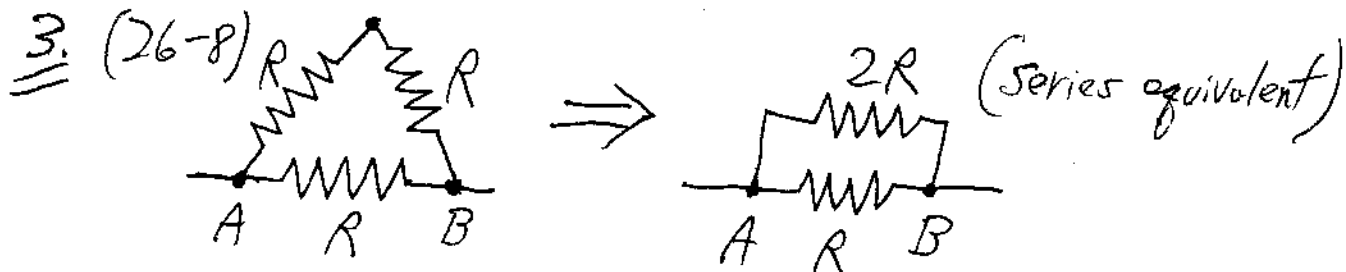1. (26-14)  $I = \frac{dQ}{dt} = \frac{25C}{0.19s} = \boxed{130A}$



$$\Delta V_t = \mathcal{E} - Ir = 1.50V - (2.33A)(0.025\Omega) = \boxed{1.44V}$$



$$\text{Now } \frac{1}{R_{II}} = \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R} \Rightarrow R_{II} = \boxed{\frac{2R}{3}}$$

4. (26-24) Use  $R = \frac{\rho l}{A}$  and  $\rho = \rho_0 [1 + (T - T_0)\alpha]$

Doubling diameter gives  $A' = 4A \rightarrow R' = R/4$

Doubling  $l$  gives  $R' = 2R$

Raising  $T$  by  $300K$  gives  $R' = R[1 + (300^\circ C)\alpha]$

Largest  $\alpha$  for metals (Table 26.1) is  $5.0 \times 10^{-3}/^\circ C$

Thus  $R' = 2.5R$  maximum ( $R' = 1.003R$  min.)

$\rightarrow$  Greatest Change: Changing diameter by  $\times 2$ ,  $\boxed{d}$


$\rightarrow$  Least Change:  $\boxed{\text{Depends on metal}}$  (on line)

5. (26-26) #18 wire has  $d = 1.024 \text{ mm}$ ;  $r = 0.512 \times 10^{-3} \text{ m}$


Thus  $j_{\text{max}} = \frac{I_{\text{max}}}{A} = \frac{5 \text{ A}}{\pi (0.512 \times 10^{-3} \text{ m})^2} = \boxed{6 \times 10^6 \text{ A/m}^2}$

Also  $j = \sigma E$  so  $E = \frac{1}{\sigma} j = \rho j$   
 $= (1.7 \times 10^{-8} \Omega \cdot \text{m}) (6 \times 10^6 \text{ A/m}^2)$   
 $= \boxed{0.1 \text{ V/m}}$

6. (26-39)


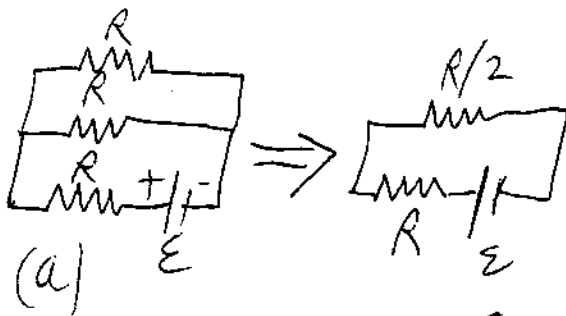

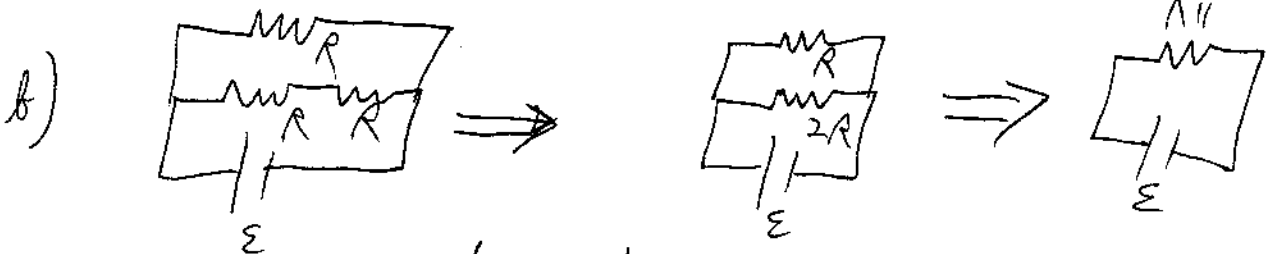
$$I = \frac{\epsilon}{R + \frac{R}{2}} = \frac{2\epsilon}{3R}$$






$$\frac{1}{R_{\text{II}}} = \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R}$$
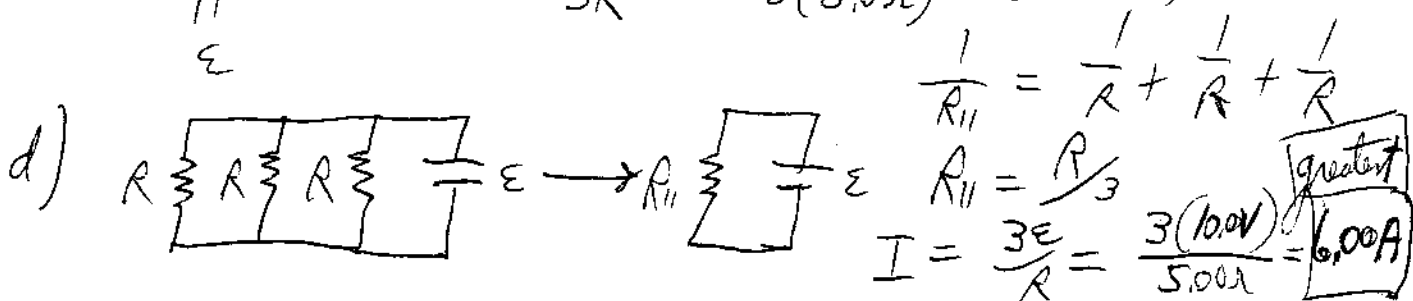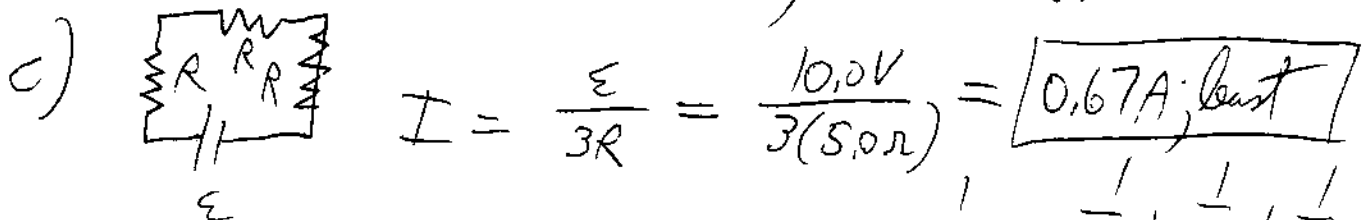
$$R_{\text{II}} = \frac{2R}{3}; \quad I = \frac{3\epsilon}{2R}$$



7. (26-43)

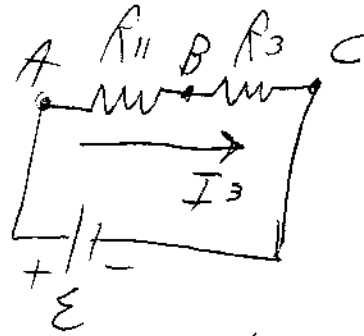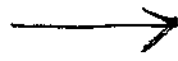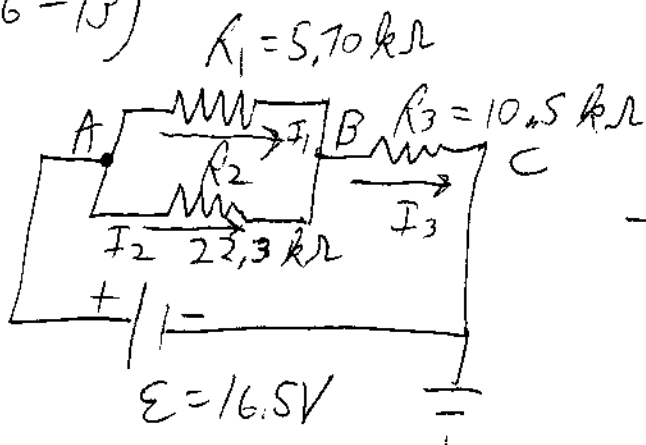

$$\frac{1}{R_{11}} = \frac{1}{5.70 \text{ k}\Omega} + \frac{1}{22.3 \text{ k}\Omega}$$

$$R_{11} = 4.54 \text{ k}\Omega$$

$$\text{Then } I_3 = \frac{\mathcal{E}}{R_{11} + R_3} = \frac{16.5 \text{ V}}{15.0 \text{ k}\Omega} = \boxed{1.10 \text{ mA}}$$

$$\text{Now } \boxed{V_C = 0}$$


$$V_B = V_C + I_3 R_3 = \boxed{11.5 \text{ V}}$$

$$V_A = V_B + I_3 R_{11} = 11.5 \text{ V} + (1.10 \text{ mA})(4.54 \text{ k}\Omega) = \boxed{16.5 \text{ V}}$$

$$\text{Also } I_1 = \frac{V_A - V_B}{5.70 \text{ k}\Omega} = \frac{5 \text{ V}}{5.70 \text{ k}\Omega} = \boxed{0.877 \text{ mA}}$$

$$I_2 = \frac{V_A - V_B}{22.3 \text{ k}\Omega} = \frac{5 \text{ V}}{22.3 \text{ k}\Omega} = \boxed{0.224 \text{ mA}}$$


8. (26-50)

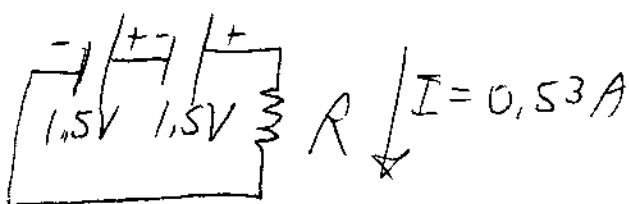

$$R = \frac{\Delta V}{I} = \frac{3.0 \text{ V}}{0.53 \text{ A}} = \boxed{5.7 \Omega}$$

$$P = I \Delta V = (0.53 \text{ A})(3.0 \text{ V}) = \boxed{1.6 \text{ W}}$$


23058-6-4

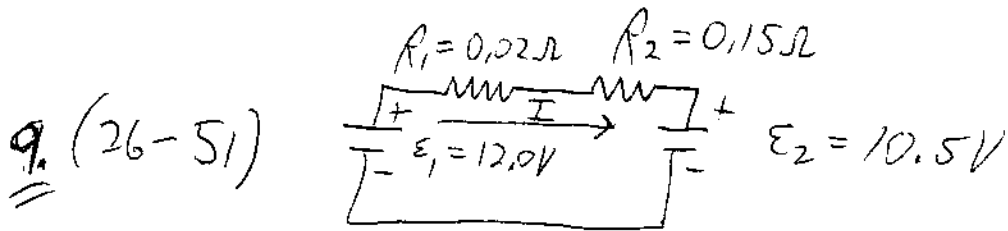

Kirchhoff loop equation gives  $\mathcal{E}_1 - I(R_1) - IR_2 - \mathcal{E}_2 = 0$

$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{1.5V}{0.17\Omega} = \boxed{8.8A}$$

10. (26-53)

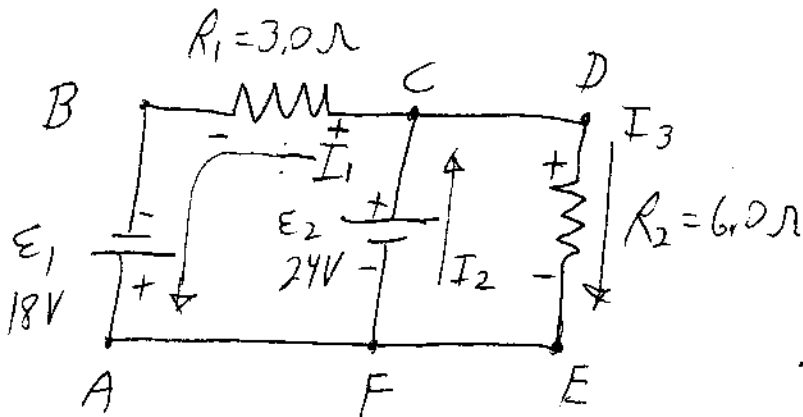

Junction equation at C:

$$I_2 = I_1 + I_3$$

Loop equation for ABCFA:

$$-\mathcal{E}_1 + I_1 R_1 - \mathcal{E}_2 = 0$$

$$I_1 = \frac{\mathcal{E}_1 + \mathcal{E}_2}{R_1} = \frac{42V}{3.0\Omega}$$

$$= \boxed{14A}$$

Loop eqn for ABCDEFA

$$-\mathcal{E}_1 + I_1 R_1 - I_3 R_2 = 0$$

$$I_3 = \frac{I_1 R_1 - \mathcal{E}_1}{R_2} = \frac{14A(3.0\Omega) - 18V}{6.0\Omega}$$

$$\text{from junction eqn } I_2 = I_1 + I_3 = \boxed{4A} + \boxed{14A} = \boxed{18A}$$