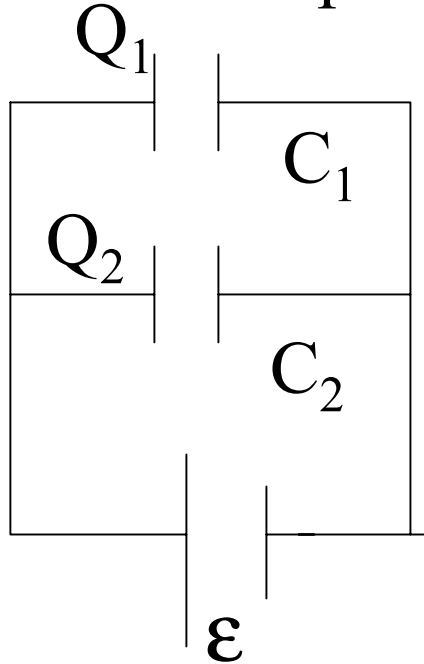


Combinations of Capacitors

- Parallel capacitors



$\Delta V = \varepsilon$ same for C_1 and C_2

$$\Delta V = Q_1/C_1 = Q_2/C_2$$

Total stored chg. $Q = Q_1 + Q_2$

Total capacitance is :


$$C_{\parallel} = \frac{Q_{total}}{\Delta V} = \frac{Q_1 + Q_2}{\Delta V} = C_1 + C_2$$

- Same for any number of capacitors in parallel, so

$$C_{\parallel} = \sum_i C_i$$

- Adding capacitors in parallel similar to increasing plate area

Series Capacitors

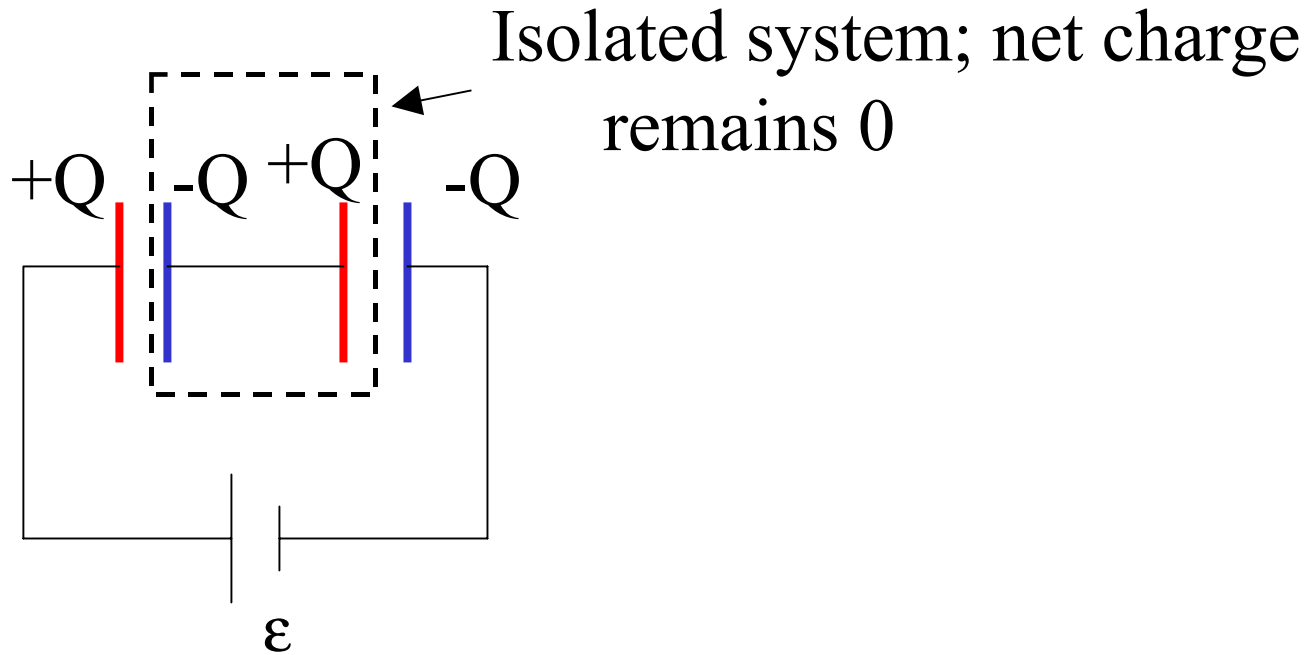


- Each of the series capacitors will have the same charge

$$\varepsilon = \Delta V = \Delta V_1 + \Delta V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{Q}{C_s}$$

- Thus

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} = \sum_i \frac{1}{C_i}$$

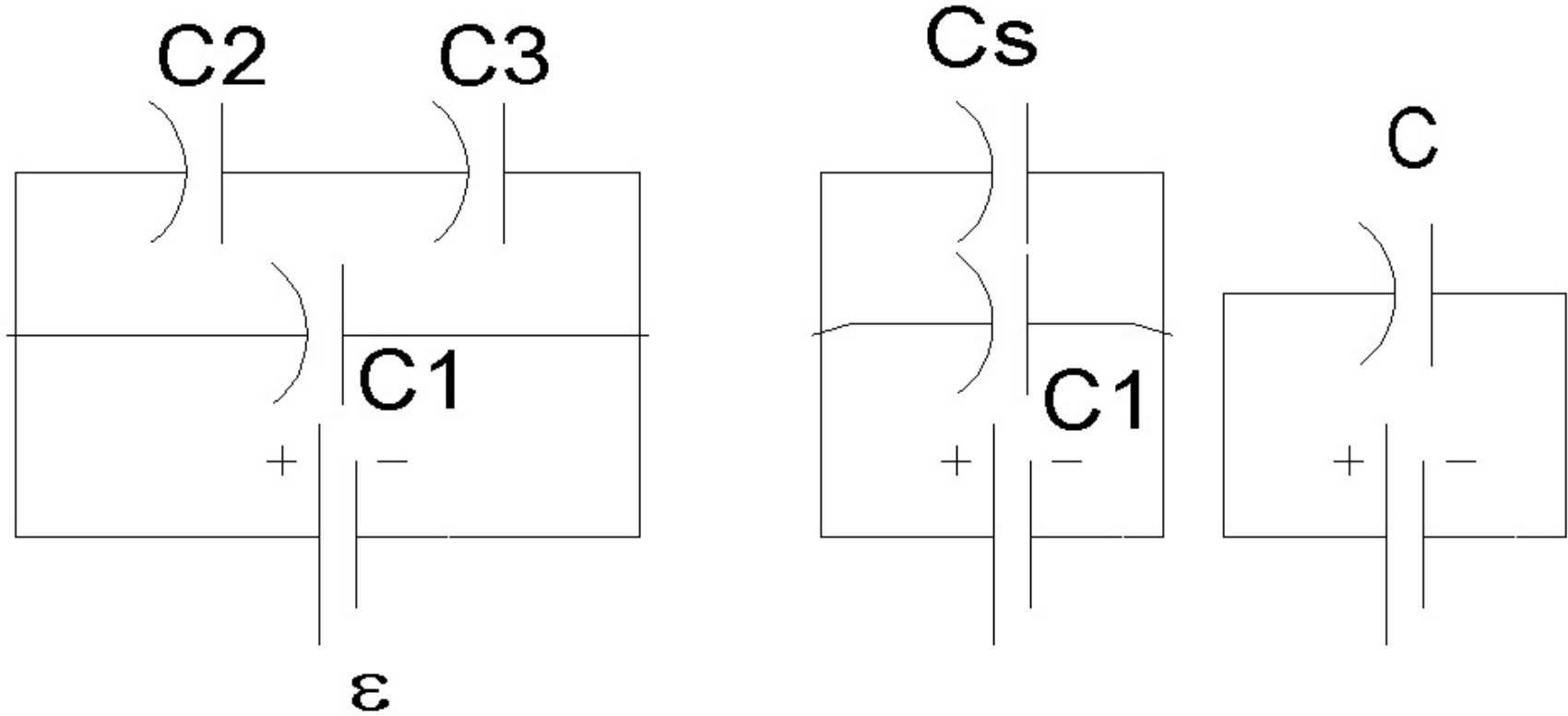
- Note that series capacitors combine like parallel resistors and vice versa
- Q1: Capacitance of $6\mu\text{F}$ and $3\mu\text{F}$ capacitors in series?



$$\frac{1}{C_s} = \frac{1}{C_2} + \frac{1}{C_3} \dots\dots\dots C = C_s + C_1$$

$$Q_3 = Q_2 = Q_S = C_S \varepsilon$$
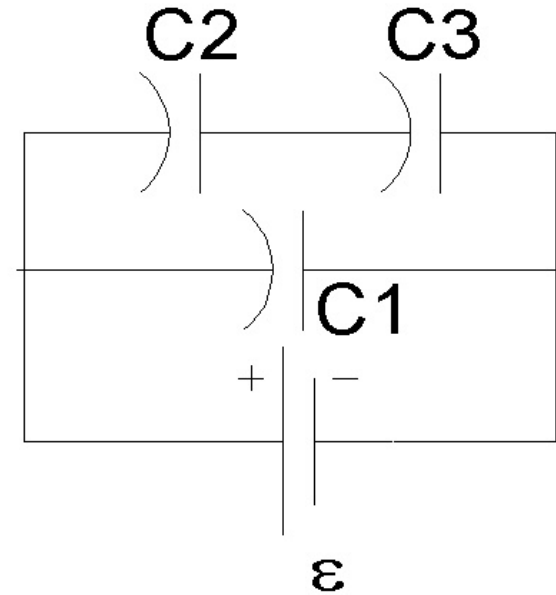
$$C_S = \left(\frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$



$$\Delta V_2 + \Delta V_3 = \varepsilon$$

$$Q_2 = Q_3 = Q \Rightarrow C_2 \Delta V_2 = C_3 \Delta V_3 = C_S \varepsilon$$

$$\Delta V_3 = \frac{C_S}{C_3} \varepsilon$$


$$U_3 = 0.5 C_3 (\Delta V_3)^2$$

$$= 0.5 Q_3^2 / C_3$$



Dielectric Material in Capacitors

(Electric Fields in Materials)

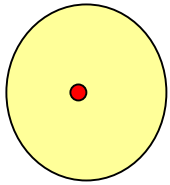- Dielectric is an insulating material whose atoms or molecules can be *polarized*




Neutral,
unpolarized atom

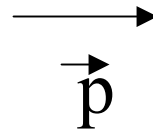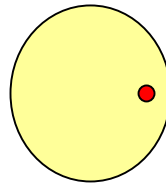

Polarized atom; still neutral, but
applied electric field produces
dipole moment \vec{p}

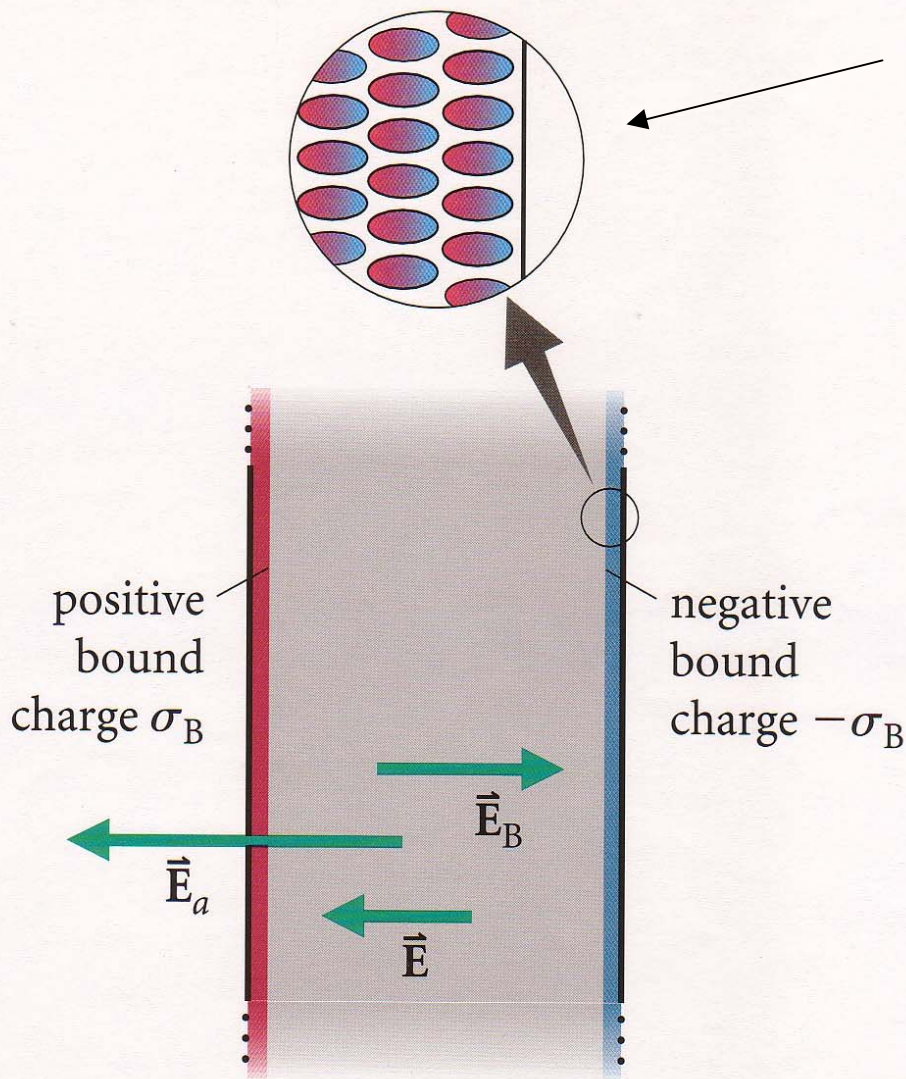- Charge in the polarized atom is *bound* - not free to move. In a block of polarized material, bound charge cancels out except at surfaces:



In interior of block,
bound charge cancels out.

Left with sheet of
positive bound surface
charge & sheet of
negative bound surface
charge

Applied field strength E_A

Field of bound charge E_B

Net field $E = E_A - E_B$ is
smaller than E_A

\vec{E}_a applied external field

\vec{E}_B field produced by bound charge

$\vec{E} = \vec{E}_a + \vec{E}_B$ total field within the material

Dielectric Constant κ

- Describe effect of material on electric field in terms of material's dielectric constant κ (dimensionless)


$$\kappa \equiv \frac{|\vec{E}_A|}{|\vec{E}|}$$

- Some values of κ :

Vacuum	1.0000
Air	1.0006
Polyethylene	2.4
Mylar	3
Alum. Oxide	11

Dielectric in a Capacitor

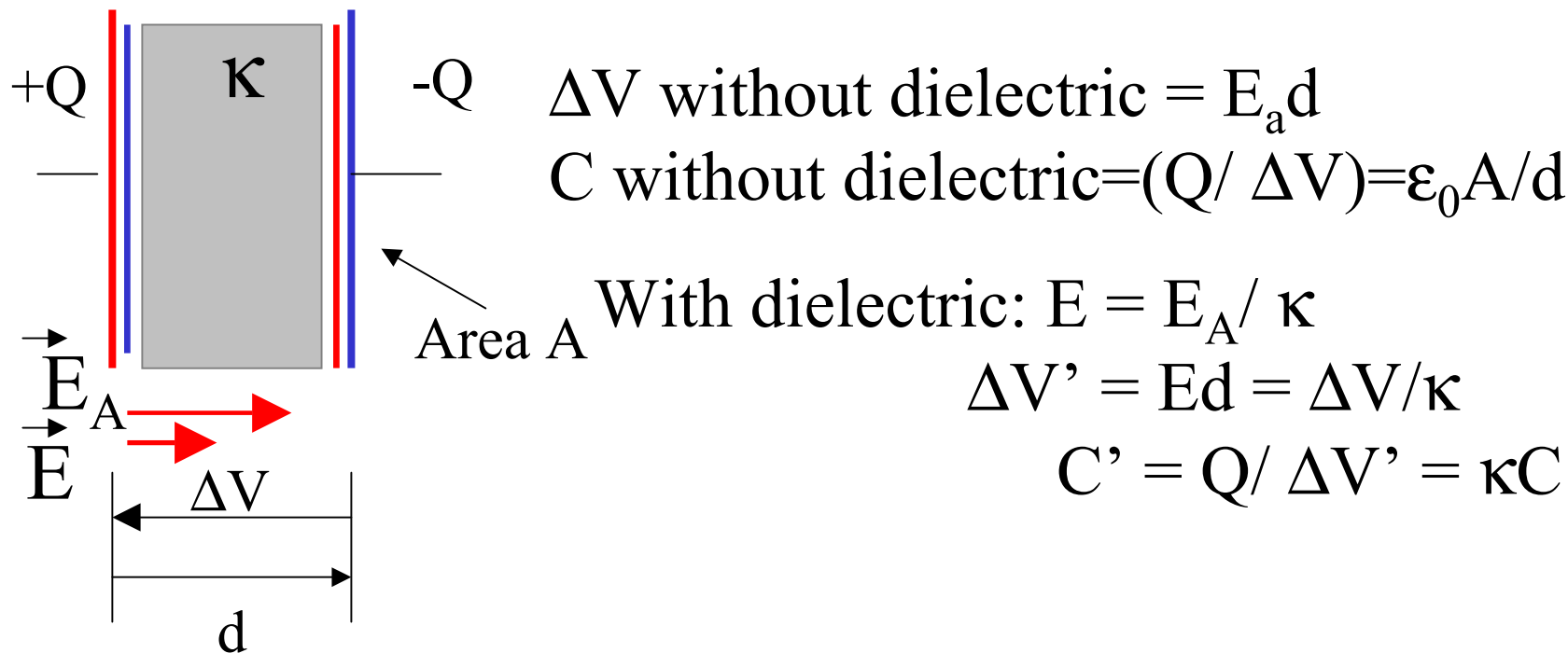- If we fill space between capacitor plates with material of dielectric constant κ , then for a given charge on the capacitor, the electric field between the plates is reduced, the potential difference between the plates is smaller, and the capacitance is larger:



Effect of Dielectric on Capacitance

- Capacitance C' with dielectric in terms of capacitance C without dielectric: $C' = \kappa C$
- Example: what is capacitance of parallel plate capacitor with 0.5 m^2 plates $8.85 \times 10^{-4} \text{ m}$ apart with Mylar dielectric ($\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$)? (Q3)